 


Transistors :- Semiconductor device can be used to conduct electric current.



⇒ BJT (Bipolar Junction Transistor)

Base :- Used to activate the transistor.


Collector :- Positive Lead

Emitter :- Negative Lead.



⇒ FET (Field Effect Transistor)

Gate, Source and Drain

 


Voltage at Gate controls the current between source and drain.

MOSFET Transistors


(Metal-oxide-semiconductor field-effect transistor)

PMOS & NMOS Transistors

 

When $x=0$

There is conducting path from S to D

 

When $x=1$

There is a conducting path from S to D

PMOS v/s NMOS ?

Bistable Latching Circuitry

(flip-flop) to store each bit.

Static RAM :-

→ Semiconductor memory was flip-flops to store each bit.


→ Can be arranged in rows and columns of memory cells.

Word line and bit line

→ Widely used in small-scale systems like microcontrollers


→ Cache Memories

1-bit SRAM Cell

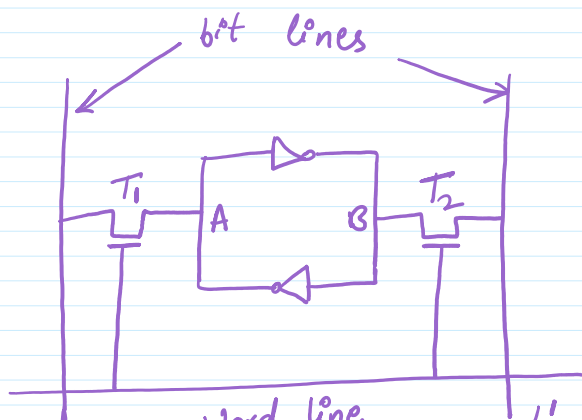


2 pass transistors

4 transistors for inverter pair.

 

- Two inverters are cross connected to form a latch
- Connected to two bit lines with T_1 and T_2
- Transistors behave like switches that can be (OFF) and (ON) under the control of word line.

Read operation :-

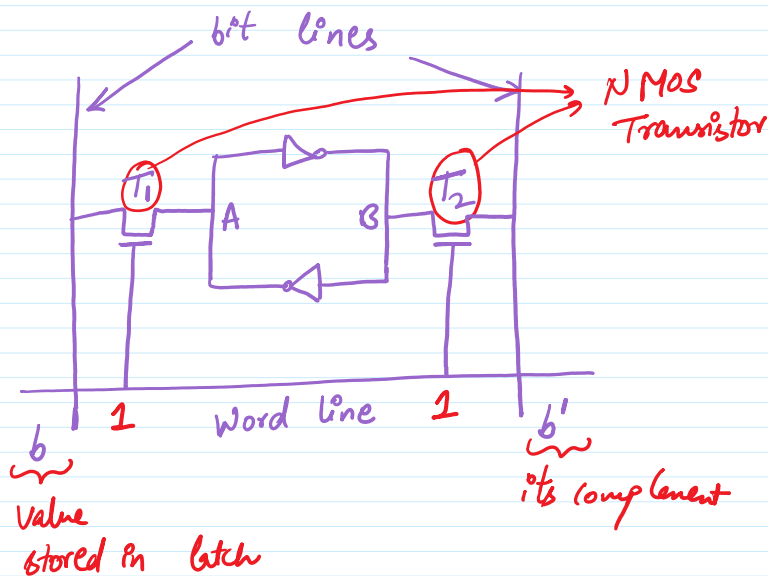

- ① To read content of the cell, word line is activated (= 1) $\Rightarrow T_1 \rightarrow ON$
 $T_2 \rightarrow ON$

If value is 1 bit-line (b) $\rightarrow 1$
bit-line (\bar{b}) $\rightarrow 0$


If value is 0 $b \rightarrow 0$
 $\bar{b} \rightarrow 1$

Read / Write signal will monitor the state

of b and \bar{b} to figure out value (0/1)

Write operation:-

Write 1
Write 0

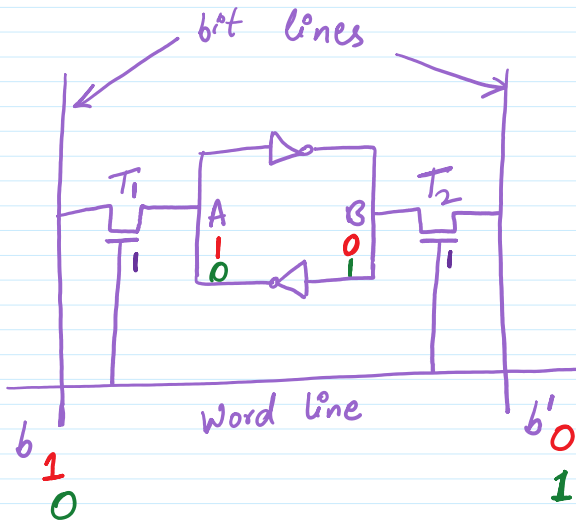


Dynamic RAM:-

→ Do not retain its state even if power supply is ON.

→ Data stored in the form of charge stored on a capacitor.

1-transistor DRAM Cell

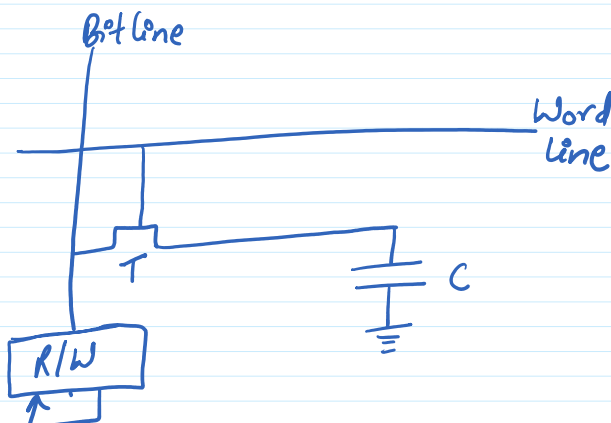




→ Requires periodic refresh
(due to leakage in charge)

→ Less expensive.

⇒ READ Operation in DRAM

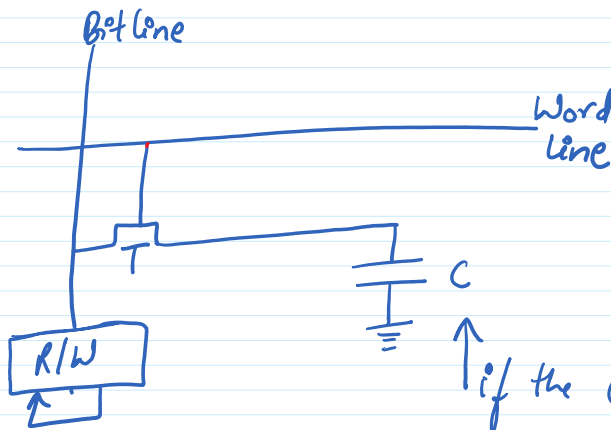

→ The transistor of a particular cell is turned on by activating the word line


→ R/W control signal will sense the charge stored in the capacitor.

↑ if the charge is above threshold,
⇒ high voltage with logic 1

if below threshold, grounded logic 0.


⇒ WRITE Operation in DRAM

To be written:—
0, 1

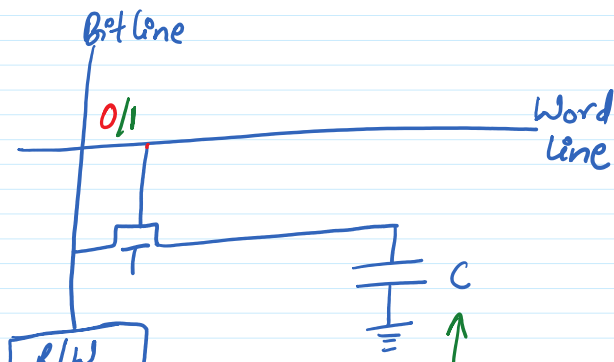

→ Word line → transistor

 → Depending on the value to be written, (0/1) apply voltage (high/low)




apply voltage (high/low)

The capacitor gets charged to the required voltage state.

⇒ Refreshing of capacitor requires READ-WRITE cycles.

Types of DRAM

 

→ Timing of memory is handled asynchronously.

A special memory controller.

→ Memory operations are synchronized by a clock.